

بسم الله الرحمن الرحيم  
التاريخ : 2009 /1/26  
الزمن : ساعتان

المادة/ اقتصاد هندسي  
( EE21111 )  
الفرقة الثانية (لائحة قديمة)

جامعة طنطا  
كلية الهندسة  
قسم الالكترونيات والاتصالات الكهربائية

أجب عن الأسئلة الآتية:- (30 درجة)

السؤال الأول:-

- 1- " هناك العديد من انواع التكاليف تستخدم في الاقتصاد الهندسي عند تحليل الجدوى المالية للمشروعات الصناعية" تكلم بالتفصيل عن انواع التكاليف.
- 2- تكلم عن اهم الخطوات الرئيسية للدراسة الاقتصادية .
- 3- اشرح بالتفصيل العناصر الاساسية لتصنيع منتج ما.

السؤال الثاني:-

- 1- اكتب نبذة متصرة عن:-  
التكاليف - سياسة الاحتكار - المنفعة الكلية والحدية
- 2- ما هي العوامل التي تؤثر على الطلب.
- 3- اقترض شخص ما مبلغ 20000 جنيه على ان يسدد المبلغ بعد 12 سنة بفائدة مركبة 8% احسب المبلغ الذي يلزم سداه في نهاية المدة.

السؤال الثالث:-

- a. ما هي العناصر الاساسية لتكلفة منتج ما.
- b. ما اهمية دراسة الجدوى الفنية للمشروعات- مع شرح لاهم المسائل التي تعالجها دراسات الجدوى الفنية.

مع أطيب التمنيات بالنجاح  
د/د.عبد الفتاح مصطفى خورشيد

المادة : رياضيات هندسية (أ)  
 الزمن : ٣ ساعات  
 الفرقة : الثانية (إتصالات- لائحة قديمة)  
 تاريخ الإمتحان : ٢٨ / ١ / ٢٠٠٩ (الفصل الأول)

جامعة طنطا  
 كلية الهندسة  
 قسم الفيزيكا والرياضيات الهندسية

**Answer the questions [ 85 Mark ]**

**Question 1 [40 Mark]**

1-a ) Fit the readings

x	1.00	1.25	1.5	1.75	2.00	2.25
y	1.12	0.92	0.75	0.61	0.51	0.42

for the exponential curve  $y = b e^{ax}$

1-b ) In an examination the number of students who obtained marks between certain limits were as follows :

Marks	0 - 19	20 - 39	40 - 59	60 - 79	80 - 99
No. of students	41	62	65	50	17

Estimate the number of students who obtained less than 70 marks.

1-c) Evaluate  $\int_4^{5.2} \ln x \, dx$  correct to 6 decimal by using Simpson s Rule .

1-d) Obtain the estimate of the missing figures in the following table

x	2.0	2.1	2.2	2.3	2.4	2.5	2.6
f(x)	0.135	--	0.111	0.100	--	0.082	0.074

**Question 2 [ 45 Mark]**

2-a) Find the value of y at  $x = 2.6$  by using modified Euler s Methods with  $h = 0.2$ , if  $y = \sqrt{x^2 + 4y^2}$  ,  $y(2.2) = 1.5$

2- b ) Using Gauss - Seidel Method , solve the system of linear equations  
 $5x_1 - x_2 + 3x_3 = -2$  ,  $x_1 + 5x_2 - 2x_3 = 10$  ,  $2x_1 - 4x_2 + 10x_3 = 6$

2-c ) Use the finite difference method with  $n = 4$  to approximate the solution of the boundary - value problem

$$y'' + 6.55(x + 1)y = 1 \quad , \quad y(0) = 0, \quad y(1) = 0$$

Answer the following questions:


- 1- a- Find the Z- parameters of the T-network that has  $Z_a = 8 \Omega$ ,  $Z_b = 10 \Omega$ , and  $Z_c = 12 \Omega$ .  
b- Find the ABCD parameters of the ideal transformer that has turns ratio of 10 : 4.  
c- Find the input impedance of the ideal transformer that is given in (1-a) when it is loaded by a capacitor of 10 micro Farad.
- 
- 2- a- Find the Y-parameters of the  $\pi$ -network that has  $Y_1 = 0.4 \text{ mho}$ ,  $Y_2 = j 0.4 \text{ mho}$ , and  $Y_3 = -j 0.3 \text{ mho}$ .  
b- A Common Emitter Amplifier has the parameters,  $h_{re} = 0$ ,  $h_{ie} = 200 \Omega$ ,  $h_{fe} = 100$ , and  $h_{oe} = 100 \mu \text{ mho}$ . Also  $R_E = R_L = R_C = 800 \Omega$ ,  $R_1 = 1.3 \text{ k} \Omega$ ,  $R_2 = 2.7 \text{ k} \Omega$ ,  $R_S = 2 \text{ k} \Omega$ , and  $C_E = C_i = C_o = 20 \mu \text{ Farad}$ . Calculate the input impedance, voltage gain, and the current gain.
- 
- 3-a- Show how you could use the operational amplifier to integrate the following inputs:  
 $V_a = 5 \sin \omega t$ ,  $V_b = 5 t$ ,  $V_c = 5$   
b- A five bits A/D converter with resolution 0.5, and  $R_F = 0.35 \text{ LSB resistance}$ . Determine the output voltage when the input voltage is "11010".
- 
- 4 - Draw the logic circuit of the following functions, and minimize them,  
 $F_1 = C + AB\bar{C} + AB$   
 $F_2 = ABC\bar{D} + A\bar{B}C\bar{D} + AB\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D}$
- 
- 5- a- Simplify the functions:  
 $F_1 = \sum 0, 1, 2, 3, 4, 6, 7, 8, 12, 13$   
 $F_2 = \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$   
 $F_3 = \bar{A}C + \bar{A}B + A\bar{B}C + BC$   
b- Compare between calculating the value of the following function as Sum of Products and as Product of Sum;  
 $F = \bar{A}\bar{B} + \bar{A}B + A\bar{B} + AB$

**Answer the following questions:**

- Q1:** a) Explain the properties of the system and give an example for each (at least four).  
b) Write five groups of the signals and give an example for each.

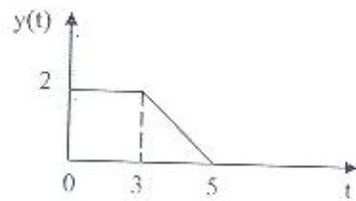**Q2:** Given the following signals:

$$x(t) = u(t) - u(t-2) + u(t-5) - u(t-6)$$



- Write  $y(t)$  in terms of singularity functions
- Sketch the signal  $x(t)$
- Calculate the energy and the power for the signal  $y(t)$

**Q3:** a) Find  $y(t)$  for the following systems:


$$1) \frac{Y(s)}{R(s)} = \frac{4}{s^2 + 6s + 5}$$

$$2) \frac{Y(s)}{R(s)} = \frac{s+2}{s^2 + 4s + 13}$$

for the input is unit step signal.

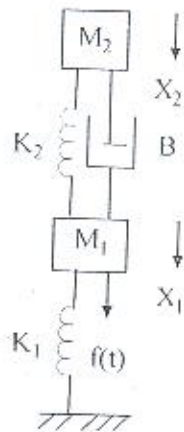b) For the mechanical system shown below, find the following

- Write the differential equations of performance.
- Determine the transfer function  $X_2(s)/F(s)$ .




(انظر الصفحة التالية)

Q4: a) Calculate the Fourier Series for the signal

$$x(t) = 4 \cos\left(\frac{\pi}{2}t + \frac{\pi}{4}\right)$$


b) For the following system:

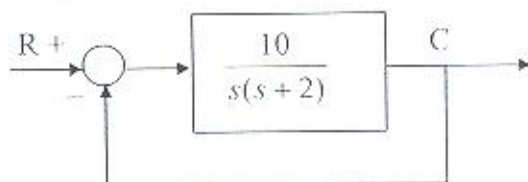

- 1) Determine the natural frequency and damping factor?
- 2) Compute the percentage overshoot for the step input?

Q5: Determine the transfer function of the system using:

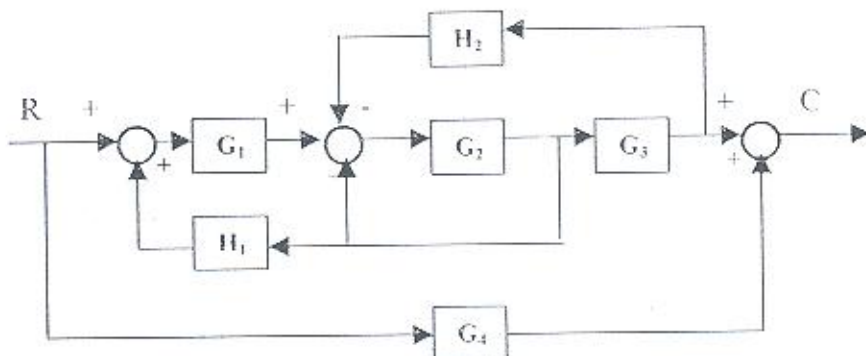- a) Block diagram reduction.
- b) Signal flow graph.



مع أطيب الأمنيات بالتوفيق والنجاح

Answer All The Following:

1-a-) Draw the circuit diagram of a class B power amplifier, showing the input and output waveforms.

b-) What is meant by "Push-Pull". Draw the circuit diagrams of the two common approaches for using push-pull amplifiers to reproduce the entire waveform.

c-) The n and p-channel E-MOSFETs that are shown in Fig. 1 has a threshold voltage of +0.2 V, and -0.2 V respectively. What resistance setting for  $R_6$  will bias the transistors to class AB operation. At this setting, What power is delivered to the load if the input signal is 100 mV(rms). You may consider that potentiometer  $R_1$  is set to 440 $\Omega$ .

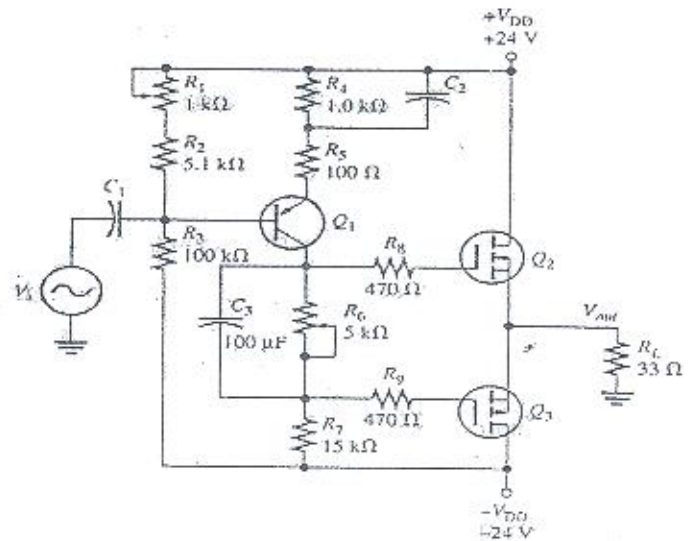


Fig. 1

2-a-) Drive an expression of the input resistance, output resistance, and voltage gain of the noninverting amplifier using ideal op-amp. If  $R_1=3\text{ K}\Omega$ ,  $R_2=43\text{ K}\Omega$ , and  $V_s=0.1\text{ V}$ , find the output voltage, output current, and the voltage gain of the noninverting amplifier.

b-) Design a noninverting amplifier to have a closed loop gain of 35 dB, and an output resistance of no more than 0.2  $\Omega$ . The only op-amp available has an output resistance of 250  $\Omega$ . What is the minimum open loop gain of the op-amp that will meet the design requirements.

3-a-) An op-amp differentiator with 1.5msec time constant is driven by a waveform shown in Fig. 2. Draw the output waveform of the differentiator.

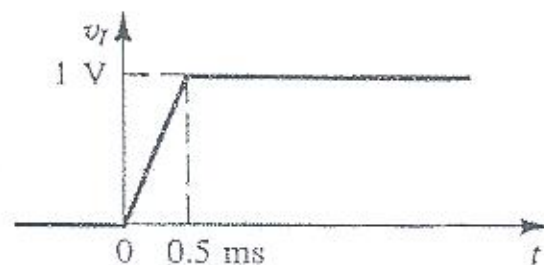


Fig. 2

b-) Design a low pass filter to have an input resistance of 10 K $\Omega$ , midrange gain of 10, and a bandwidth of 20 KHz.

P.T.O

c-) For the instrumentation amplifier shown in Fig. 3, if  $V_1=2.5V$ ,  $V_2=2.25V$ ,  $R_1=R_3=15\text{ K}\Omega$ ,  $R_2=150\text{ K}\Omega$ , and  $R_4=30\text{ K}\Omega$ . Find the values of  $V_o$ ,  $V_a$ , and  $V_b$ .

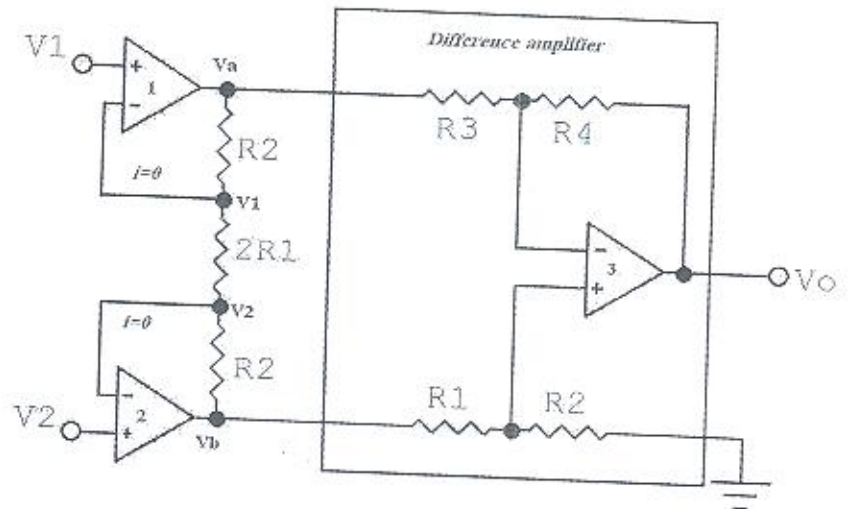


Fig. 3

4-a-) Draw the circuit diagram of the Wien bridge oscillator. Drive an expression for the frequency of oscillations.

b-) Draw the circuit diagram of the phase shift oscillator using three lag circuits. Prove that the frequency of oscillations of the oscillator is  $f_r = \frac{1}{2\pi\sqrt{6RC}}$ .

5-a-) Draw the circuit diagram of the CB Colpitts oscillator. Drive an expression for the feedback ratio, and the voltage gain needed to start oscillations.

b-) Calculate the oscillating frequency for the oscillator shown in Fig. 4. Assume that, there is negligible loading on the feedback circuit and that its Q is greater than 10. What is the frequency of oscillations if the Q drops to 8.

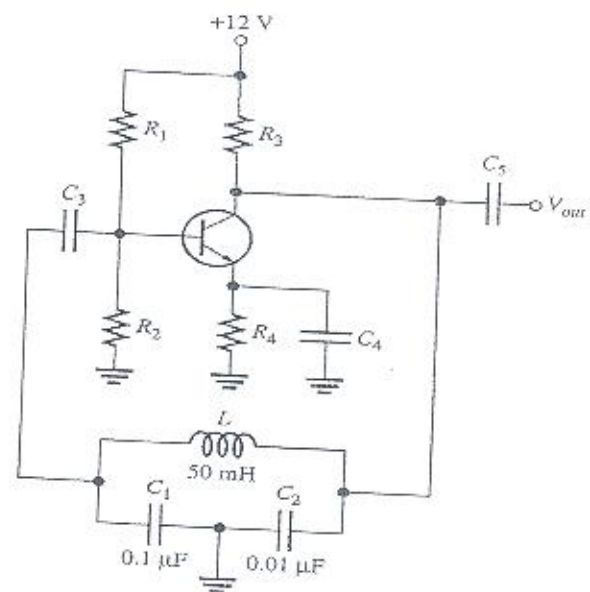


Fig. 4

c-) Draw the schematic diagram of the VCO. If  $R_1=75\text{ K}\Omega$ ,  $R_2=30\text{ K}\Omega$ , and  $C=47\text{ nF}$ . What are the frequency and duty cycle when  $V_{con}=1\text{ mV}$ .

Best Wishes  
Said Elhalafawy

**Solve the following problems:**

[1] The op amp in Fig. 1 is ideal.

- Find the range of values for  $\alpha$  in which the op amp does not saturate.
- Find  $i_o$  (in microamperes) when  $\alpha = 0.12$ .

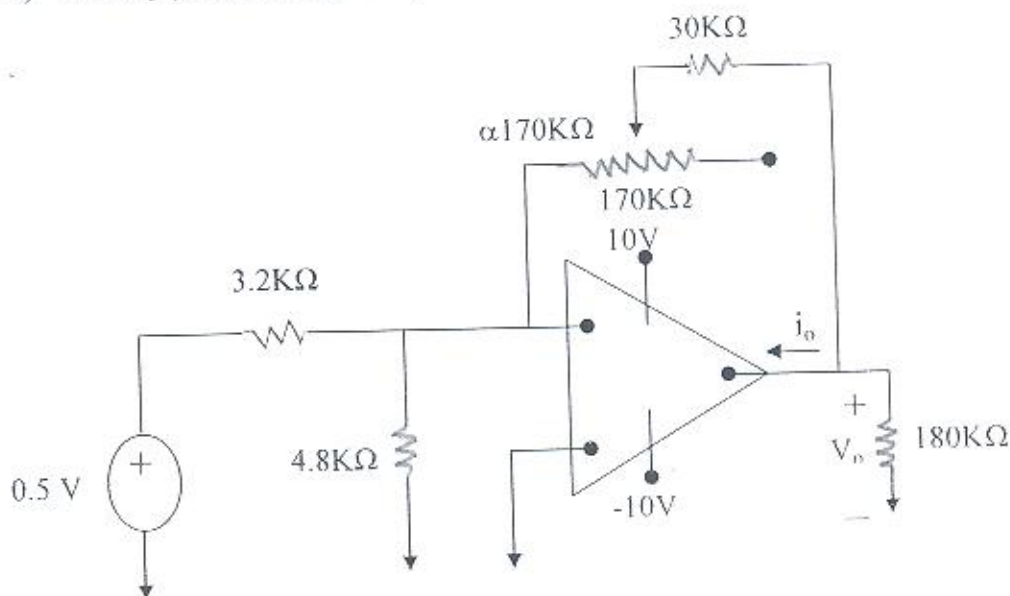


Fig. 1

[2] The switch in the circuit in Fig. 2 has been in position a for a long time. At  $t=0$ , the switch moves instantaneously to position b.

- Find  $i_o(t)$  for  $t \geq 0^+$ .
- What percentage of the initial energy stored in the capacitor is dissipated in the  $3\text{ K}\Omega$  resistor  $500\ \mu\text{s}$  after the switch has been moved to position b.

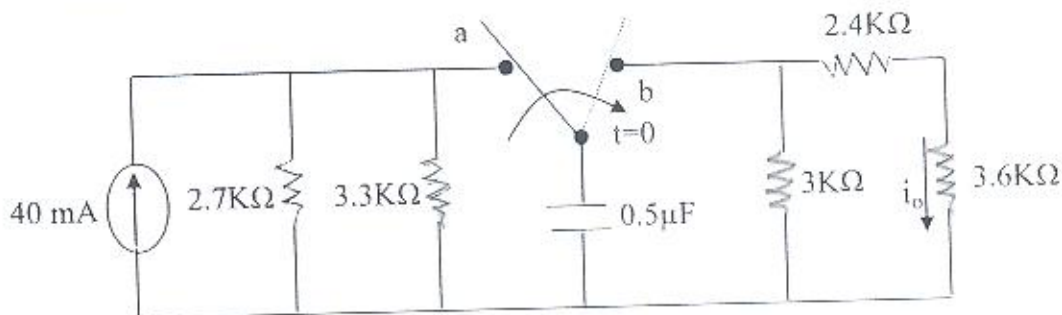


Fig. 2

[3] The switch in the circuit in Fig. 3 has been closed a long time. At  $t=0$  it is opened. Find  $v_o(t)$  for  $t \geq 0^+$ .



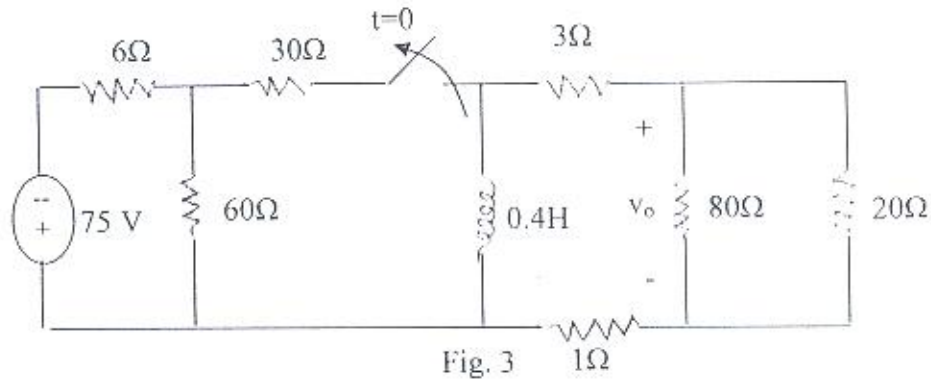


Fig. 3

- [4] The switch in the circuit in Fig. 4 has been open a long time before closing at  $t=0$ . It is opened. Find  $i_1(t)$  for  $t \geq 0$ .

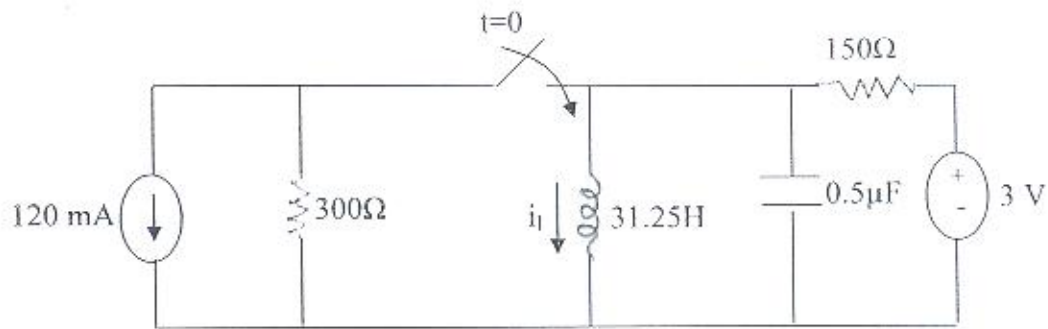


Fig. 4

- [5] The switch in the circuit in Fig. 5 has been in position 1 for a long time. At  $t=0$ , the switch is moved instantaneously to position 2. Find  $i(t)$  for  $t \geq 0$ .

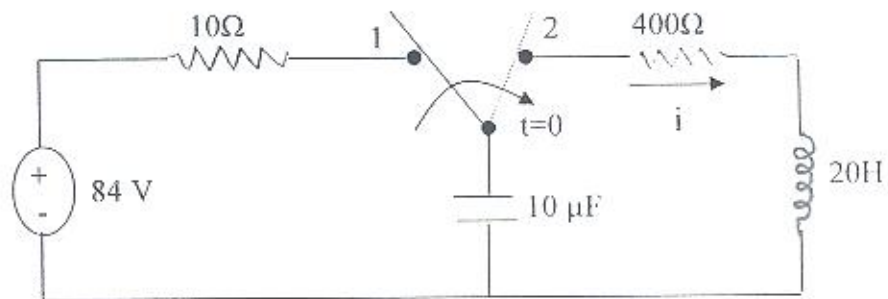


Fig. 5