



امتحان تخلفات 2014/2015

Second year: Electrical Power and Machines Engineering

Total Marks: 120

Course Title: Electrical Machines (1)

Time: 3 hour

Date: June , 2015

Code: EPM2208

**Question 1:**

**Marks[20]**

State **true** or **false** and correct the false statements rationally.

**a- Each of the following points equals 1 marks**

- 1- A Long shunt compound generator, fitted with Interpoles, is commutatively compound. If supply terminals unchanged and the machine runs as a motor, it will be differentially compound.
  - 2- The frequency of armature current depends only on speed.
  - 3- The increase of brush resistance enhances commutation and voltage regulation.
  - 4- The external generator characteristic is a relation between induced EMF and armature current.
  - 5- Each equalizing ring connects a number of conductors equals number of poles.
  - 6- The resultant pitch of retrogressive lap windings is positive odd number.
  - 7- Number of parallel paths of wave windings is equal to the number of pole pair.
  - 8- The critical resistance of series generator is the summation of armature and field resistance.
  - 9- Iron losses are found in stator only while copper losses are found in stator and rotor.
  - 10- Increase of armature inductance enhances the commutation.
- b- A 2-poles DC generator with simple 2-layer lap winding with 6 armature coils, Determine:
- 1- Number of commutator segments
  - 2- Front pitch, back pitch and commutator pitch.-
  - 3- Draw the development winding and show the brush position.

**[10 Marks]**

**Question 2:**

**Marks[20]**

- a- Draw the laboratory circuit connection(s), with suitable measurements instruments, and the equivalent circuit that is used to determine the no load characteristics of shunt generator. Define all used symbols. Suggest a table of results. Draw the relevant



runs at 800 rpm taking a current of 100 A. What must be the resistance of a diverter connected across the armature to reduce the speed to 500 rpm. Assume the armature current to be constant. **[10 Marks]**

[b] A 500 V, 45 kW, 600 rpm DC shunt motor has a full load efficiency of 95%. The field resistance is 300 Ohm, and armature resistance is 0.4 Ohm. Find the speed under each of the following conditions at which the motor will develop an electro-magnetic torque equal to  $\frac{3}{4}$  of rated value:

- (i) Regenerative braking: no limiting resistance.
- (ii) Plugging: external limiting resistance of 8.5  $\Omega$  inserted.

The field current is maintained constant and armature reaction and the brush drop are neglected. **[10 Marks]**

**Question 6:**

**Marks[20]**

[a] Aided with neat illustration(s) and equation(s), explain in details, Swinburne's test for determining the efficiency of a DC machine. Explain briefly how the efficiency can be found in brake test. **[10 Marks]**

[b] A 220 V, 15 kW shunt motor has a maximum efficiency of 90% and a speed of 1000 rpm when delivering 90% of its rated output. The shunt-field resistance is 100 Ohm. Determine the efficiency and speed when the motor draws a current of 110 A from the mains. **[10 Marks]**

*Dr. Mohamed El-Nemr*

*Dr. Abdelsalam Ahmed*

**REPETED- EXAMINATION 2014/2015 Power Electronics (1)**



*Electrical Power and Machines Engineering  
Department*



**TANTA UNIVERSITY**

**Faculty Of Engineering**

**REPETED- EXAM.2014/2015**

<b>Course</b>	<b>Power Electronics (1)EPM2209</b>	<b>Time</b>	<b>3 hours</b>
<b>Students</b>	<b>2<sup>nd</sup> Year Electrical Power and Machines Engineering</b>	<b>Mark</b>	<b>100</b>
<b>Date</b>	<b>16/5/2015</b>	<b>No. of Pag.</b>	<b>1</b>

Answer ALL the following questions:

**The first question (25 marks)**

- A Discuss briefly the effect of gate current of SCR on its anode current
- B A single-phase half wave rectifier is used to charge a battery of 60V and 300 W-H. If the supply voltage is 110 V, find
  - (a) The diode conduction angle;
  - (b) The charging time in hours;
  - (c) The value of current limiting resistor for 10A (DC current) flows through battery;
  - (d) The power loss through the current limiting resistor; and
  - (e) The circuit efficiency.

**The second question (25 marks)**

- A Drive an expression for the reduction of the output voltage due to the source inductance effect for three-phase uncontrolled rectifier.
- B Three-phase full-wave uncontrolled rectifier is supplied from star connected supply of 380 V, 50Hz. The load current is 50 A and a negligible ripples, calculate.
  - (a) the reduction of output voltage due to commutation if the source inductance is 0.4 mH /phase
  - (b) the average and rms of diode current;
  - (c) the input power factor;
  - (d) the transformer utilization factor; (e) the PIV of diodes

**The third question (25 marks)**

- A How can you protect SCR from di/dt and dv/dt?
- B Single-phase semiconverter is used to feed a highly inductive load with resistance of 5 ohm. If the supply voltage is 220 V and converter delay angle is  $60^\circ$ , determine:
  - (a) Average and r.m.s value of output voltages;
  - (b) the average and r.m.s value of output currents;
  - (c) the average and r.m.s value of thyristor currents;
  - (d) the rectifier efficiency and ripple factor of input current;

**The fourth question (25 marks)**

- A What are the methods used to improve the system power factor? And discuss briefly the extinction angle control method?
- B Single phase series full converter is connected to feed a highly inductive load with ripple free average load current and resistance 30 ohm. The supply voltage is 220 V and  $N_p : N_s = 2:1$ . If the average output voltage is 70 % of the maximum possible average output voltage, calculate:
  - (a) the delay angles of the converters;
  - (b) the rms and average load voltage of the converter;
  - (c) the rms and average SCR currents;
  - (d) the input power factor and TUF.

Good Luck and best wishes Dr. Abdelwahab Hassan