

جامعة طنطا

كلية الهندسة

قسم هندسة إلكترونيات
قسم الاتصالات الكهربائية

يونيو ٢٠٠٧

استحارة بقرار دراسات بيئية

الفترة الثانية (اللاحة قديمة)

الزمرة المهندس

أجب عن الأسئلة التالية :

- ١- أذكر أهم مصادر التلوث بالموجات الكهرومغناطيسية والآثار السلبية الناتجة عنه مثل هذا النوع من التلوث.
- ٢- اكتب عن الطرق المختلفة لتوليد الطاقة الكهربائية وقارن فيما بين هذه الطرق فيما يخص استهلاك الموارد البيئية والتلوث البيئي المصاحب لكل وحدة من المنتج.
- ٣- اذكر الاستراتيجيات البيئية الخاصة بإقامة محطات توليد المحمول.
- ٤- اكتب مذكرة وافية عن مصادر الطاقة الجديدة والمتجددة.
- ٥- اكتب مذكرة وافية عن طرق رفع كفاءة استخدام مصادر الطاقة التقليدية لضمان استدامة الموارد البيئية المتجددة في إنتاجها.
- ٦- اكتب مذكرة وافية عن مساهمة القدرة وتأثيرات وطرق تحسينه ومزود ذلك على ترسيدها واستخدامها في توليد الطاقة الكهربائية.
- ٧- اكتب مذكرة وافية عن المجالات الكهرومغناطيسية الناتجة عن المحولات والمعدات الثقيلة ومخطوط نقل الطاقة الكهربائية مع إعطاء أمثلة.
- ٨- اشرح مخطط يوضح تسلسل العمليات في محطة توليد الطاقة الكهربائية باستخدام الطاقة المتجددة وماهي أهم المعدات المستخدمة في توليد الطاقة الكهربائية.

TANTA UNIVERSITY
Faculty of Engineering
Power Engineering and Electrical Machines Department

Course : Electromagnetic fields
Code : EPM2104
Year : 2nd
Date : 15 / 1 / 2007

Exam : Final
Time : 3 Hours
Department : Power Engineering
& Electrical Machines

Answer All Questions:

Question(1)

- a) Using Gauss's law. Derive the electric flux density due to a uniform line charge distribution ρ_l C/m lying along the z axis and extending from $-\infty$ to $+\infty$
- b) Determine the electric field intensity \mathbf{E} at point P(2,0,0) due to three standard charge distribution:
 - i) A uniform surface charge at $x = -2$ m with $\rho_s = -0.2$ nC/m²,
 - ii) A uniform surface charge at $x = 5$ m with $\rho_s = +0.2$ nC/m²,
 - iii) A uniform line charge at $x = 8$ m with $\rho_l = 4$ nC/m.

Question(2)

- a) Derive the two characteristics of the relationship between potential difference V and electric field intensity E at any point. Also write down the voltage gradient equation in spherical coordinates.
- b) For the potential field $V = 2x^2y - 5z$ in free space, evaluate at point P(-4,3,6):
 - i) The potential
 - ii) The magnitude and direction of the electric field intensity
 - iii) The electric flux density
 - iv) The volume charge density.

Question(3)

- a) Aided with sketches derive the boundary conditions at surface separating two dielectrics having permittivities ϵ_1 , ϵ_2 . Derive the relation between electric field intensities \mathbf{E}_1 and \mathbf{E}_2 and electric flux densities \mathbf{D}_1 and \mathbf{D}_2 in terms of θ_1 , ϵ_1 , ϵ_2 , and θ_2 .
- b) Find the relative permittivity of the dielectric material used in a parallel plates capacitor if:
 - i) The capacitance, $C = 40$ nF, separation distance, $d = 0.1$ mm, and surface area, $S = 0.15$ m²
 - ii) Electric field intensity, $E = 500$ kV/m, and $\rho_s = 10$ μ C/m².
 - iii) Electric flux density, $D = 50$ μ C/m² and the energy density is 20 J/m³.

Question(4)

- a) Using Ampere's circuital law derive a mathematical expressions for the magnetic field intensity \mathbf{H} from $\rho = 0$ to $\rho = \infty$ of an infinitely long coaxial transmission line carrying a uniformly distributed total current I in the inner solid conductor and $-I$ in the outer hollow conductor, given that the inner solid conductor radius is h and the hollow outside conductor inner radius is b and its outer radius is c, where $h < b < c$. Sketch H versus ρ from 0 to ∞ .
- b) A filamentary conductor carries current of 10 A is directed from infinity to the origin along the positive x axis and then back out to infinity along the positive y axis. Use Biot-Savart law to find the magnetic field intensity \mathbf{H} at P(0,0,1).

TANTA UNIVERSITY

Faculty of Engineering [Final Exam, Jan. 2006-2007]

Course: Energy Conversion

2nd Year (Dept. Electric Power & Machines Eng.)

Old Curriculum

Time: 3 hours

ملاحظات عامة: لا يحوز عن أي من هذه أو غيرها قيمتها (المعروفة) بل ترك الاجابة بدلا منهما
الفرص رموزا او قوما والقيمة لاي معطيات لم تذكر و تحتاجها
وضح اجابتك بشكل توضيحي مرسومة بعبارة ومعادلات كلما امكن ذلك

Attempt all questions

من فضلك لاحظ ان درجات الاسئلة مختلفة

Question 1

a For the machine shown in Fig. 1, derive an expression for the mutual inductance between the two windings taking the fundamental component of stator flux density.

(10 points)

b For a slotted armature: i) sketch the flux lines in a slot. Show that there is little force on conductors in slots. ii) show that there is a strong force exerted on the iron teeth by deriving an expression for the mechanical torque applying the principle of conservation of energy. For this purpose, assume no change in stored energy and no electrical or mechanical losses.

(5 points)

Questions 2

Fig. 2 shows a section a section of a machine having two identical stator windings aa' , bb' , in quadrature. The self inductance of the each stator winding is L_{sa} and the rotor wing is L_{sr} and they are constants independent of θ_s . The mutual inductance between a stator winding and the rotor winding is a function of the angular position of the rotor as follows: $M_{sr} = M \cos \theta_s$; $M_{sr} = M \sin \theta_s$, where M is the maximum value of the mutual inductance. The rotor winding is excited with dc I_r . The rotor is revolving at a synchronous speed so that its instantaneous angular position is given by $\theta_s = \omega t - \delta$. The resistance of each of the stator phases is r and that of the field winding is r_f . Derive expressions for the open circuited terminal voltage of each coil in terms of the given data.

(10 points)

Question 3

a Draw a developed sketch of winding that produce a pulsating mmf in rotating machine. Show by equations that such mmf can be decomposed into two rotating mmf's.

(5 points)

b Derive an expression for the torque developed by a cylindrical synchronous motor having two poles similar to that shown in Fig. 2 but without the winding bb . The rotor windings are excited with dc current I_r , while the stator winding is connected to an ac source with current $i_a = \sqrt{2} I_m \cos \omega t$. L_{sa} and M_{sr} may be assumed as in question 2.

(i) Write an expression for the energy stored in terms of ω and angular position θ_s .
(ii) What is the rotor speed ω_r at which an average torque will be produced?
(iii) Find the average torque.

(15 points)

Question 4

- a For a singly excited translational system, derive expressions for current, flux linkage, force in the form of stored energy or coenergy. (15 points)
- b Show that the energy stored in a rotating magnetic system given by $W_s(\lambda, \theta) = \int_0^{\lambda} i(\lambda, \theta) d\lambda$ regardless of how λ varies with θ . Hint: Integrate $d\lambda$ over a two-section path: one with $\lambda = 0$ and the other with $\theta = \text{constant}$. (5 points)
- c Prove an expression for the differential force that acts on a current carrying conductor of differential length dl placed in a magnetic field of density B tesla. (5 points)

Question 5

- a State with illustrations three different types of the collectors used with applications of solar electric energy. (10 points)
- b Draw a sketch of a domestic application that uses solar heat energy. (10 points)

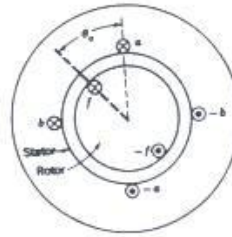
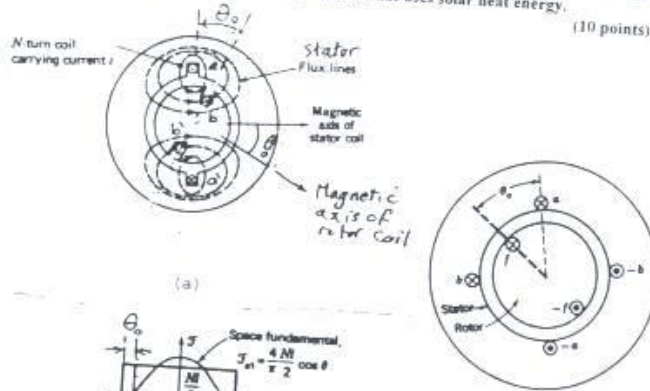


Fig. 2

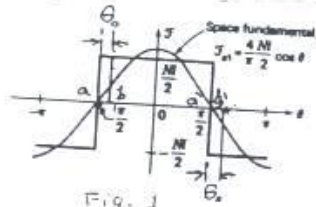


Fig. 1

END OF EXAM

LUCK ◀ GOOD ▶ BYE

Answer the following six questions:

Q(1): For the circuit in Fig. Q1

a) Prove that $V_o = \frac{R_b}{R_a} (V_b - V_a)$ when $\frac{R_a}{R_b} = \frac{R_c}{R_d}$

b) For $\frac{R_a}{R_b} = \frac{R_c}{R_d} = \frac{1}{5}$, $V_b = 4.0 \text{ V}$ and $V_{cc} = 10 \text{ V}$,

what range of values for V_a will result in linear operation?

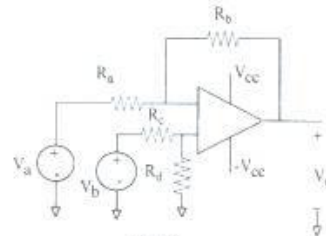


Fig. Q1

Q(2): The voltage pulse described by the following equations is impressed across the terminals of $0.5 \mu\text{F}$ capacitor:

$$V(t) = 0 \quad t \leq 0$$

$$V(t) = 4t \quad 0 \leq t \leq 1$$

$$V(t) = 4 e^{-(t-1)} \quad 1 \leq t \leq \infty$$

- Derive the expressions for the capacitor current, power, and energy.
- Specify the interval of time when energy is being delivered by the capacitor.

Q(3): a) Deduce the current response for an RL circuit with step voltage source.

b) The current source in the circuit generates the current pulse shown in Fig. Q3.

There is no energy stored at $t = 0$.

1- Derive the numerical expressions for $v(t)$ for the time intervals $t < 0$, $0 < t < 40 \mu\text{s}$, and $40 \mu\text{s} < t < \infty$

2- Calculate $v(60 \mu\text{s})$ and $v'(60 \mu\text{s})$

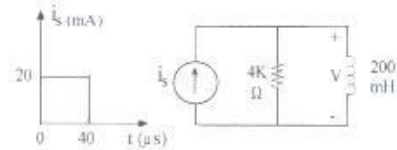


Fig. Q3

Q(4): The switch in the circuit shown in Fig. Q4 has been in position **a** for a long time.

At $t = 0$ the switch is thrown to position **b**. Find

a) V_c for $t \geq 0$

b) $i(t)$ for $t \geq 0^+$

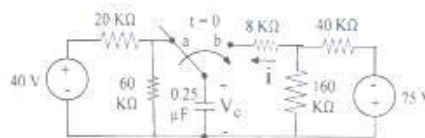


Fig. Q4

Q(5): The uncharged capacitor in the circuit shown in Fig. Q5 is initially switched to terminal **a** of the three position switch. At $t = 0$ the switch is moved to position **b**, where it remains for 20 ms. After the 20 ms delay, the switch is moved to position **c**, where it remains indefinitely.

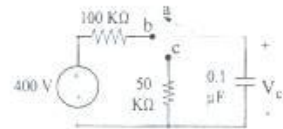


Fig. Q5

- Derive the numerical expression for the voltage across the capacitor.
- Plot the capacitor voltage versus time.
- When will the voltage on the capacitor equal 200 V ?

Q(6): The initial energy stored in the circuit in Fig. Q6 is zero. At $t = 0$, a dc current source of 24 mA is applied to the circuit.

- What is the initial value of I_L and dI_L/dt ?
- What is the numerical expression for $I_L(t)$ when $t \geq 0$?

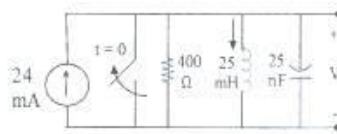


Fig. Q6

Answer the following questions :-

1-a) Consider the one – dimensional heat equation $u_t = u_{xx}$, $0 \leq x \leq 1$, $t \geq 0$
 with the boundary conditions $u(0,t) = 0$, $u_x(1,t) = 1$

Compute the first two rows of the solution if $h = \frac{1}{3}$, $k = \frac{1}{18}$

and the initial condition $u(x,0) = x$.

1-b) Use Euler's method to find y' at $x=0.2$, 0.4 , if $y'' = 4yy' + xy$, $y = 2$
 and $y' = 1$ at $x=0.1$.

2-a) Evaluate $\int_4^{5.2} \ln x \, dx$ correct to 6 decimal by using Simpson's rule .

2-b) Find $f(0.7)$ from the following readings

x	0.4	0.6	0.8	1
y	0.3799	0.537	0.664	0.7616

3-a) Fit the curve $y = a + bx$ to the readings

x	0.5	1.0	1.5	2.0	2.5	3.0
y	0.31	0.82	1.29	1.85	2.51	3.02

and find the root mean square of the errors .

3-b) Use the simple iteration method to obtain the smallest positive root
 of the equation $x^3 - 8x + 5 = 0$ correct to five decimal places .

3-c) By the use of Gauss – Seidel method solve the system of linear equations
 $5x_1 - x_2 + 3x_3 = -2$, $x_1 + 5x_2 - 2x_3 = 10$, $2x_1 - 4x_2 + 10x_3 = 6$

4-a) To what degree of accuracy can we calculate $\sqrt{115}$ by means
 of Lagrange's interpolation formula for the function $y = \sqrt{x}$ if we choose
 the interpolation $x_0 = 100$, $x_1 = 121$, $x_2 = 144$?

4-b) From the following table , find the number of students who obtained less than 45 marks

Marks	30 - 40	40 - 50	50 - 60	60 - 70	70 - 80
No. of St	31	42	51	35	31

المادة: الاقتصاد الهندسي	المقابلة الضلع الهندسة الأول	ليه الهندسة
السنة: الثانية (حاجيات + إحصائيات)	٢٠٠٦ / ٢٠٠٥	باسم منكم
الترتيب: حافق	يناير ٢٠٠٦	د/التقارير الهندسية

جيب عمدة الأسئلة الآتية:-

السؤال الأول

- اذكر العناصر المطلوبة لإتمام مشأة صناعية؟
- اسر مع أثره الإنتاج؟
- اسر مع اسر مع ثمره العوائق المتناقصه؟
- عامل يتأخر ١٢ جنيه لكل ساعة لتاد إنتاج 2٥ قطعة بالساعة على آلة تبلغ تكلفته ١٠٠ ريال؟
- عامل يتأخر ٧٥ جنيه بالساعة فإذا وجد على آخر أقل تفوقاً منه الأول بمقدار ١٨ ساعة فإنه صاحب التكاليف الأعلى للقطعة الواحدة من كلاً إلى ليشه ثم احب التكاليف عند ما يتوزع العمل على عاملين ينتج ١٠٠ قطعة بالساعة وما هي الملاحظات التي يمكن أن تستنتجها؟

السؤال الثاني

- اذكر ما تعرفه من الطبع والوصف والرونة؟ ثم وضع العزم بين حدوده الطبع ورونة الرسم؟
- اسر مع اسر مع مؤثر الخبز والنظا؟
- ما هو المبلغ الذي يجب ايداعه في 1 يناير ١984 لكل ١٠٠٠ دولار بعد ذلك حتى 1 يونيو ١992 كمن يتم سحب 1٥٥٥ جنيه كل ١٠٠٠ دولار لمدة 5 سنوات بتأخر 1 يناير ١993 ٩ الربيع الاكس هو 11% مع التكميل لوقت السنوي؟ اسر مع القاذبه مره من المثل ثم الجدول مره اخرى في المثل؟

السؤال الثالث

- اذكر فوائده حساب التكاليف؟ ثم وضع بالشكل عناصر التكاليف؟
- اسر مع اسر مع ضريبة التقاعد؟
- اقتصد مصنع ما مبلغ 2٥٥٥٥ جنيه لتفادته لبيعه قدرها 1٥% سنوياً والتفقد مع الدائم عن مداواة فدون خمس سنوات والمطلوب توضيح خلوها السداد مستوداً كلاً من طرفه مختلفه؟

تاسع تولى

آلات كهربائية - طابعت

TANTA UNIVERSITY	Course: Electrical Machines
Faculty of Engineering	2nd Year
Dept. of Computer & Control Eng	Time: Three hours

FINAL EXAM. 2005-2006

Question 1

- Explain how is eddy-current loss in transformers affected by magnitude and frequency of the applied voltage. How can it minimized?
- By giving reason(s) مع ذكر الاسباب للتدعيم الاجابة mention what will happen the machine laboratory when the mechanical load is removed completely while a dc series motor is running.
- Aided with ONE equation ONLY, suggest three methods for speed control of dc motors. State the effect(s) of varying each parameter the speed. غير مطلوب اي رسومات
- Using a variable frequency source to control the speed of a three phase induction motor, if the voltage is kept constant, what will be effect on the machine flux? What is (are) the limitations of frequency reduction? Verify your answer with equation(s).
- Draw ONLY diagram(s) to show how the direction of rotation of squirrel-cage induction motor can be reversed.
- Draw coil connection diagram(s) of a phase of three phase induction motors to show how the number of poles can be changed. What effect does this have on the operating speed.
- Suppose that, for a given excitation and load, a synchronous motor draws a unity pf current. The load is then kept constant while excitation is increased. Aided with a phasor diagram, discuss change in the power factor and armature current.
- Aided with illustration(s), explain the basic construction and principle of operation of a selsyn.
- Aided with illustration(s), explain three applications of lift motors.

Question 2

The parameters of the equivalent circuit of a 150 kVA, 2400 V/240 V transformer, are $r_1 = 0.2 \text{ Ohm}$, $r_2 = 2 \text{ Ohms}$, $x_1 = 0.45 \text{ Ohm}$, $x_2 = 4.5 \text{ Ohms}$, $R_c = 10 \text{ k. Ohms}$, $X_m = 1.55 \text{ k. Ohms}$. Using the approximate equivalent circuit referred to the primary, determine the (a) vol

regulation and the efficiency of the transformer operating at rated load with 0.8 lagging power factor.

Question 3

In a long-shunt compound generator, the terminal voltage is 230V when generator delivers 150A. Determine i) the induced e.m.f. ii) total power generated iii) distribution of this power, given that: shunt field series field, diverter and armature resistances are 92, 0.015, 0.03 and 0.032 Ohms respectively.

b) A 250- V, dc shunt motor draws a full-load line current of 100 A at the rated speed of 1200 r/min. The armature circuit resistance R_a is 0.1 ohm and the field winding resistance is 250 ohm;. Determine (a) the gross full-load mechanical power output, (b) the electromagnetic torque developed at full load, and (c) the speed regulation, if the no-load armature-winding current is 10 A.

Question 4

A 2300-V, 3-phase, wye-connected, round-rotor synchronous motor has $x_s = 2$ Ohm per phase and $R_a = 0.1$ Ohm per phase. The motor operates at 0.866 leading power factor while taking a line current of 350 A. Find the rms value of the induced phase voltage, the power angle, and the developed and maximum torque.

Question 5

A 3-phase slip-ring motor has negligible stator-winding resistance, the total leakage reactance referred to the rotor being 5 Ohms per phase and the rotor-winding resistance 0.45 Ohm per phase. When running with slip rings short-circuited and exerting full load torque the slip is 3%. Determine (i) the external rotor resistance per phase to give full load torque at starting, and (ii) the external rotor resistance per phase to give a stable speed of 50% of synchronous speed with a torque of 50% of full load torque.

END OF EXAM

LUCK ◀GOOD▶ BYE

TANTA UNIVERSITY
Faculty of Engineering
Power Engineering and Electrical Machines Department

Course : Electromagnetic fields	Exam : Final
Code : EPM2142	Time : 3 Hours
Year : 2 nd	Department : Electronics and
Date : 15 / 1 / 2007	& Communications

Answer All Questions:

Question(1)

- a) Using Gauss's law. Derive the electric flux density due to a uniform line charge distribution ρ_l C/m lying along the z axis and extending from $-\infty$ to $+\infty$
- b) Determine the electric field intensity \mathbf{E} at point P(2,0,0) due to three standard charge distribution:
 - i) A uniform surface charge at $x = -2$ m with $\rho_s = -0.2$ nC/m²,
 - ii) A uniform surface charge at $x = 5$ m with $\rho_s = +0.2$ nC/m²,
 - iii) A uniform line charge at $x = 8$ m with $\rho_l = 4$ nC/m.

Question(2)

- a) Derive the two characteristics of the relationship between potential difference V and electric field intensity E at any point. Also write down the voltage gradient equation in spherical coordinates.
- b) For the potential field $V = 2x^2y - 5z$ in free space, evaluate at point P(-4,3,6)
 - i) The potential.
 - ii) The magnitude and direction of the electric field intensity.
 - iii) The electric flux density.
 - iv) The volume charge density.

Question(3)

- a) Aided with sketches derive the boundary conditions at surface separating two dielectrics having permittivities ϵ_1, ϵ_2 . Derive the relation between electric field intensities \mathbf{E}_1 and \mathbf{E}_2 and electric flux densities \mathbf{D}_1 and \mathbf{D}_2 in terms of $\theta_1, \epsilon_1, \epsilon_2$, and θ_2 .
- b) Find the relative permittivity of the dielectric material used in a parallel plates capacitor if
 - i) The capacitance, $C = 40$ nF, separation distance, $d = 0.1$ mm, and surface area, $S = 0.15$ m²
 - ii) Electric field intensity, $E = 500$ kV/m, and $\rho_s = 10$ μ C/m².
 - iii) Electric flux density, $D = 50$ μ C/m² and the energy density is 20 J/m³.

Question(4)

- a) Using Ampere's circuital law derive a mathematical expressions for the magnetic field intensity \mathbf{H} from $\rho = 0$ to $\rho = \infty$ of an infinitely long coaxial transmission line carrying a uniformly distributed total current I in the inner solid conductor and $-I$ in the outer hollow conductor, given that the inner solid conductor radius is h and the hollow outside conductor inner radius is b and its outer radius is c, where $h < b < c$. Sketch H versus ρ from 0 to ∞ .
- b) A filamentary conductor carries current of 10 A is directed from infinity to the origin along the positive x axis and then back out to infinity along the positive y axis. Use Biot-Savart law to find the magnetic field intensity \mathbf{H} at P(0,0,1).

University of Tanta
Department of Electrical Engineering
Electronics and Communications

Second Year
Electronic Measurements (2)

Final-Term Exam
Time Allowed: 3 Hours

Answer the following questions:

[1-a] Explain the necessary requirements that must be satisfied for a circuit to sustain oscillation. Compare between the different types of oscillators according to: (a) Circuit diagram, (b) Frequency of Oscillation, (c) Feedback Factor, and (d) Advantages and Disadvantages.

[1-b] Draw a Hartley oscillator circuit. Determine the frequency of oscillation and the minimum value of R_f to sustain oscillation for a Hartley oscillator given that: $R_i = 15 \text{ k}\Omega$, $C = 0.001 \text{ }\mu\text{F}$, $L_1 = 10 \text{ }\mu\text{H}$ and $L_2 = 270 \text{ }\mu\text{H}$.

[2-a] What are the main advantages of electronic voltmeters (EVM) compared to volt-ohm-milliameters (VOM)? Explain how does a true RMS responding voltmeter measure the RMS value of an AC waveform signal?

[2-b] Explain the main principles and two modes of operation of electronic counters and describe the types of errors associated with electronic counters.

[3-a] List three instruments that are used for frequency-domain analysis and compare between their primary functions for different applications.

[3-b] Describe the causes of harmonic distortion and how to design a distortion analyzer instrument. Compute the total harmonic distortion of a signal that contains a fundamental signal with an rms value of 10 V, a second harmonic with an rms value of 3 V, a third harmonic with an rms value of 1.5 V, and a fourth harmonic with an rms value of 0.6 V.


[4-a] State the function of a transducer and explain why transducers are important in electronic instrumentation? Explain what is meant by photoelectric transducers. Explain three different types of photoelectric transducers.

[4-b] Describe a Strain Gauge. A resistant strain gauge with a gauge factor of 2 is fastened to a steel member, which is subjected to a strain of 1×10^{-6} . If the original resistance value of the gauge is $130 \text{ }\Omega$. Calculate the change in resistance.


[5] A simple shunted ammeter with $R_m = 1500 \text{ }\Omega$ and $I_{fsd} = 100 \text{ }\mu\text{A}$ is connected in a circuit and gives a reading of 3.5 mA on its 5 mA scale. This reading is checked with a recently calibrated ammeter which gives a reading of 4.1 mA. The first ammeter gives an error because it has a faulty shunt on its 5 mA range. Calculate: The actual value of faulty shunt and the correct shunt for the 5 mA range.

Answer the following questions:

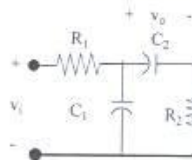Q1: a) Find the transfer function of the following system.



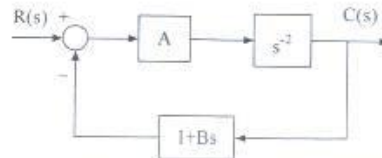b) The block diagram of a servomechanism is shown below.



Determine the value of A and B so that the peak time is 5 sec, and the maximum overshoot is 50% in unit-step response.


Q2: a) For each of the following characteristic equations, find the root distribution and determine whether the system is stable, marginally stable, or unstable:

- i) $S^3 + 8S^2 + 19S + 12 = 0$
- ii) $S^4 + S^3 + 2S^2 + S + 3 = 0$
- iii) $S^6 + S^5 + 3S^4 + 3S^3 + 2S + 1 = 0$

b) For the open loop gain $G(S)H(S) = \frac{K(S+3)}{S(S+5)(S+6)(S^2+2S+2)}$. Find

the range of K that the system is stable.

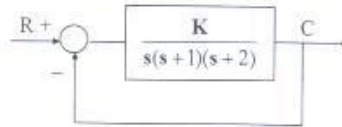Q3: For the system shown, draw the root locus plot, then determine the value of k so that the damping ration is 0.5.



Q4: a) Find a state space model for a control system having the transfer function:

$$G(s) = \frac{3(s+2)}{(s+3)(s^2+3s+5)}$$

in the pole-zero form and OCF representation.

b) Transform the following system to diagonal form.

$$\dot{\mathbf{X}} = \begin{bmatrix} 0 & 1 \\ -4 & -5 \end{bmatrix} \mathbf{X} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} \mathbf{u}$$

$$y = [1 \quad 1] \mathbf{X}$$

Then, determine whether the given system in (b) is completely state controllable and observable or not.

Q5: Sketch the Bode diagram for a system having an open loop transfer function given by

$$G(s) = \frac{200(1+0.2s)}{s(s+2)(s+10)^2}$$

then determine the gain margin and phase margin.

Attempt in all Questions

1-a) Two dielectric media with permittivities ϵ_1 and ϵ_2 are separated by a charge free boundary as shown in Fig. 1. the electric field intensity in medium 1 at P_1 has magnitude E_1 and makes an angle α_1 with the normal. Determine an expression for magnitude E_2 and direction α_2 of the electric field intensity at point P_2 in medium 2 [6 Marks]

b) Calculate the magnitude of E_2 and α_2 if $\epsilon_1 = 1$, $\epsilon_2 = 3$, $\alpha_1 = 30^\circ$, $E_1 = 1 \text{ mV/m}$ [6 Marks]

2-a) Explain with figures and equations the different types of polarization [4 Marks]

b) A narrow band signal propagates in a lossy dielectric medium which has a loss tangent 0.2 at 550 kHz, the carrier frequency of the signal. The dielectric constant of the medium is 2.5 .

i- Determine α , β , η , v_p , λ . [8 Marks]

ii- Find the distance at which the amplitude of E is 1% of its value at $x=0$ [8 Marks]

3 -) The open -circuit and short - circuit impedances measured at the input terminals of a lossless T.L of length 1.5m which is less than a quarter wavelength are $-j54.6 \Omega$ and $j103 \Omega$ respectively.

i- Find Z_0 and β of the line [5 Marks]

ii- Without changing the operating frequency, find the input impedance of a open circuited line that is twice the given length [5 Marks]

iii- How long should the short- circuited line be in order for it to appear an open circuit at the input terminals [5 Marks]

4-a) Use the smith chart to find the input impedance of a section of 50Ω lossless line that is 0.1 wavelength long and is terminated in a short circuit Repeat part a analytically. [12 Marks]

b) 50Ω transmission line is connected to a load impedance $Z_L = 35 - j47.5 \Omega$. Find the position and length of a short-circuited stub required to match the line. [15 Marks]

5-) The standing wave ratio on a lossless 50 ohm transmission line terminated in an unknown load impedance is found to be 3.0 . The distance between successive voltage minima is 20 cm , and the first minima is located at 5 cm from the load. Determine

(a) the reflection coefficient [5 Marks]

(b) the load impedance Z_L [5 Marks]

(c) The equivalent length and terminating resistance of a line such that the input impedance is equal to Z_L [5 Marks]


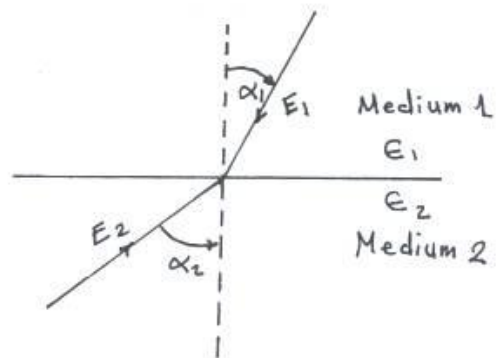


Fig. 1

Answer all the following questions (24 D. for each)

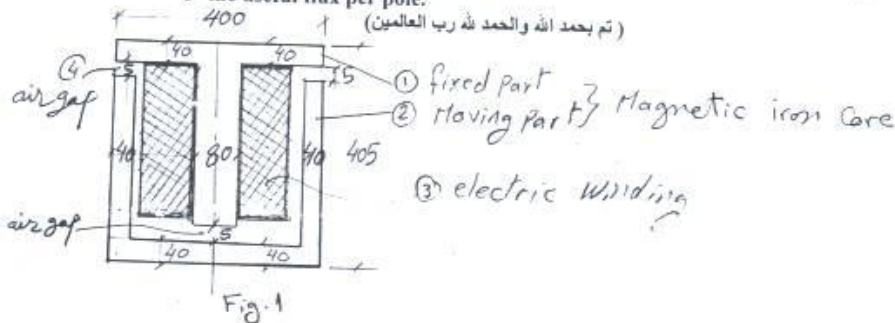- 1.) A- Explain briefly the main sources of electrical energy.
 B- What do you know about permanent magnet? A simple permanent magnet cell has a constant cross section area $A=110 / 7 \text{ cm}^2$ and an air gap $l_g = 5\text{mm}$. Calculate the permanent magnet length if the operating point on its B-H curve is $(0.8 \text{ T}, - 500 \text{ KA/m})$ and the remainder soft iron core has infinite permeability.
- 2.) A- The solar array generator can be represented as a DC supply has internal voltage V_s internal resistance r_s , draw its equivalent circuit. To obtain the V-I curve of this generator an external variable load is connected to it. If $V_s = 120 \text{ v}$, $r_s = 60 \text{ ?}$, R_l is varying as $(0, 0.5, 0.75, 1, 2, 20, 200) * r_s$, calculate the load current and voltage and then draw the V-I curve.
 B- Design a solar generator to give its optimum power transfer to the load $(60 \text{ V}, 36 \text{ A})$ where the available units of solar array has $(120 \text{ V. at no load})$ and $(2 \text{ A. at short circuit})$.
- 3.) Figure 1 shows an electromagnetic cell. All dimensions in mm and its depth is 80 mm. The flux density in all cross sectional areas are equals.
 - a- draw the magnetic equivalent circuit.
 - b- determine the m.m.f required to produce a flux density of $B= 1.4 \text{ T}$ in the iron core, if H corresponding this B from the B-H curve is 40 A/m .
 - c- calculate the magnetic force between the fixed and movable parts.
- 4.) a- Why all AC magnetic cores have laminated iron sheet.
 b- Write the stator winding factor for a distribution winding of an AC, three phase synchronous generator.
 c- A transformer has the following data;
 Primary voltage = 380 v., secondary voltage = 80 v., iron losses = 600 w, load current = 500A. at unity power factor, $r_1 = 1\text{?}$ and $r_2 = .02\text{?}$. Find:
 1- the turns ratio. 2- the transformer efficiency. 3- the secondary flux linkage.
- 5.) a- Write down the main parts of the induction motor construction and its function.
 b- A 8 Kw, 400V, 6 pole DC generator runs at 1250 rpm. If the machine has 250 conductors, lap wound and full load copper loss is 120 W. Calculate:
 1- the frequency of the induced E.M.F. 2- the induced E.M.F.
 3- the useful flux per pole.



Time allowed: 3 hours

Answer all the following questions:

Q. 1- Find the critical frequency of the input RC circuit for the FET amplifier in Fig. 1. The transistor data sheet shows that, $C_{gs} = 8 \text{ pF}$, $C_{gd} = 3 \text{ pF}$, and $g_m = 6500 \text{ } \mu\text{S}$.

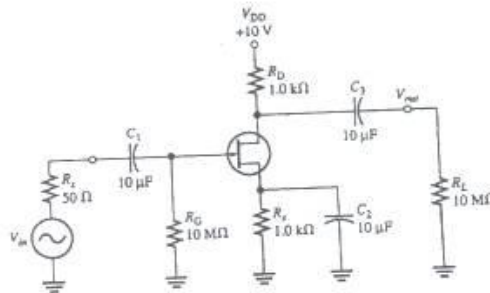


Fig. 1

Q. 2- $f_T = 200 \text{ MHz}$ is taken from the data sheet of a transistor used in a certain amplifier. If the midrange gain is determined to be 38 and if f_{CL} is low enough to be neglected compared to f_{CU} , what bandwidth would you expect. What value of f_{CU} would you expect.

Q. 3 Determine the total low frequency response of the BJT amplifier shown in Fig. 2. Draw the bode plot.

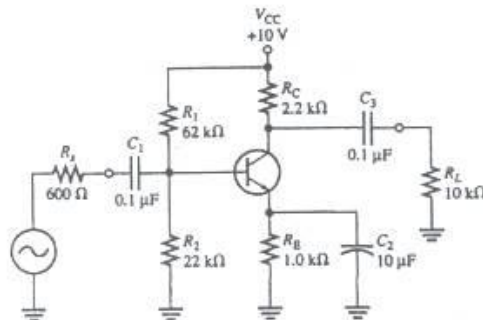


Fig. 2

Q. 4 Design a noninverting amplifier to have a closed loop gain of 35 dB and an output resistance of no more than 0.2Ω . The only op amp available has an output resistance of 250Ω . What is the minimum open loop gain of the op amp that will meet the design requirements.

Q. 5 Show that the amplifier in Fig. 3 produces an output whose magnitude is the mathematical average of the input voltages.

من فضلك اقلب الصفحة

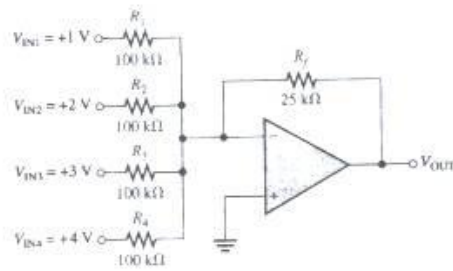


Fig. 3

- Q. 6 (a) Draw the circuit of Colpitts oscillator using FET. Find an expression for the output and feedback signals. Drive an expression for the feedback ratio, minimum gain, and frequency of oscillations of the circuit.
 (b) Determine what the gain of the amplifier stage must be in Fig. 4 in order to have sustained oscillation.

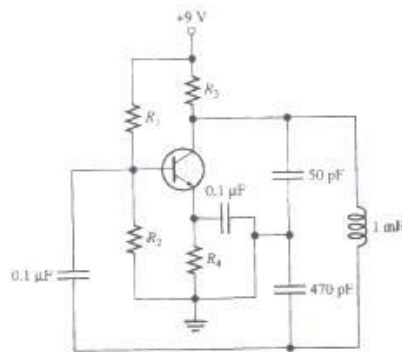


Fig. 4

- Q. 7 (a) With the aid of circuit diagram explain the operation of a monostable multivibrator. Drive an expression for LTP, UTP, and the pulse width W . Draw the schematic diagram of the monostable 555 circuit showing all connection pins on your diagram.
 (b) Determine the frequency of oscillation for the 555 astable oscillator in Fig. 5.

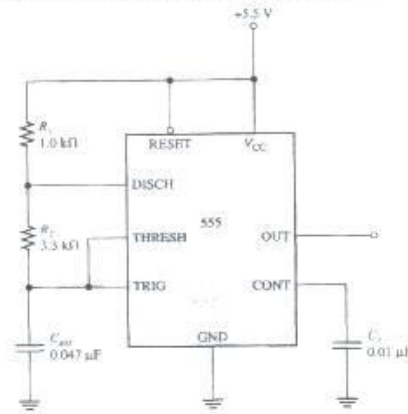


Fig. 5

Tanta University
Faculty of Eng.

Comm. Dep.

January 2007

Second Year Digital & Logic System

3.Hours

Answer should be included as you can:

{Drawing Diagram ; Truth table ; Boolean Relations}

I. Draw the electronic circuit Diagram, and realizing Truth table:

(a) 3-input OR gate (b) 4-input AND gate (c) NOT-gate (d) Tri-State Logic gate

II. Draw logic diagram for:

(a) 1-of-10 Decoder (b) 4-to-1 Multiplexer (c) 1-to-4 Demultiplexer

III. Draw Logic Diagram for:

(a) 4-bits odd parity generator (b) 4-bits Comparator (c) Decimal-to-Binary Encoder

IV. (a) Given Truth-table (fig.3.a) using Karnaugh map to derive Logic gates

(b) Draw Block Diagram for 4-bits ALU

(c) Draw logic gate for truth table (fig.3.b)

(d) Draw logic gates for truth table (fig.3.c)

V. Prove that :

(a) 3-input bubbled AND = 3-input NOR

(b) 4-input bubbled OR = 4-input NAND

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Fig(3.a)

A	Y
X	1

Fig(3.b)

A	Y
X	0

Fig(3.c)

Tanta University

Class: Second Year

Faculty of Engineering

Subject: Communication Systems

Time: 3 hours

Date: 31/5/2007

Answer the Following:

1.
 - a. Explain briefly the purposes of digitization of communication systems?
 - b. Find the value of C_{12} which will minimize the error between $f_1(t)$ and $f_2(t)$ if $f_1(t) \cong C_{12} f_2(t)$?
 - c. What are the relations between trigonometric and exponential Fourier series?
2.
 - a. Find the Fourier transform of $\sin \omega t$?
 - b. Explain the sampling theory and how to recover the signal from its Samples?
 - c. What are the characteristics of distortionless transmission systems?
3.
 - a. Define the bandwidth of a system?
 - b. Find the energy density spectrum of $f(t)$ where $f(t) = \sin \omega t$ and the duration of $f(t)$ is T ?
 - c. What is the difference between energy signal and power signal?
4.
 - a. Find the relation between output signal to noise ratio and input signal to noise ratio for Figure 1?

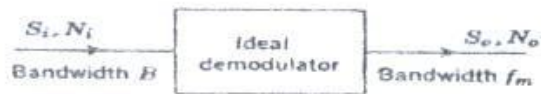


Figure 1

- b. Calculate the bandwidth of the video (picture) signal in TV, where a television picture is composed of approximately 300,000 small picture elements. Each of these elements can assume 10 distinguishable brightness levels (such as black and shades of gray) for proper contrast if we assume that for any picture element, the 10 brightness levels are equally likely to occur. There are 30 picture frames being transmitted per second. It is also given that for a satisfactory reproduction of the picture a signal-to-noise ratio of 1000 (30 db) is required.
5. a. Find the equation of the transfer function of the matched filter that maximized the signal to noise ratio at the sampling instant?
- b. Find the output of the matched filter if the present state of the input of matched filter is $\sin 200 t$ and absent state is $zero$. Calculate the optimum decision threshold value a ?
- c. Draw the structure of the optimum receiver if the present state of the input of the receiver is $s_1(t)$ and absent state is $s_2(t)$?

Dr/Mona Shokair

TANTA UNIVERSITY

Faculty of Engineering
Subject: Electronic circuits
Date: 28/12/2006

Dept. of Elec. & Comm. Eng.
Final 1ST term Exam.
Time Allowed: 3 Hours

Answer All The Following

1-a-Draw the collector characteristics of a bipolar npn junction transistor for I_B varies from 0 to $100\mu\text{A}$ with $20\mu\text{A}$ step, showing on your characteristics the value of I_C corresponding to each I_B and the three main operating regions of the transistor. Construct also the active region dc model of the transistor. You may consider that $\beta_{dc}=100$.

b-An npn transistor with $\beta_{dc}=49$ is used in common emitter amplifier circuit shown in Fig. (1) with $V_{CC}=10\text{V}$ and $R_L=2\text{K}\Omega$. If a $100\text{K}\Omega$ resistor is connected between the collector and the base of the transistor, calculate the quiescent collector current and the collector to emitter voltage drop.

2-a-Draw the ideal variation of the collector to emitter voltage and the collector current versus base current of an npn bipolar junction transistor, indicating on your graph the positions of the base and collector saturation currents.

b-What is the output voltage across the load resistor of Fig. (2) if $\beta_{dc}=\beta_{ac}=200$. Ignore r_c in your calculations.

3-a-Draw the equivalent circuit of the common emitter BJT using r-parameters. Drive an expression for the ac emitter resistance of the transistor.

b-Calculate exactly the voltage gain of the emitter follower shown in Fig. (3). If $\beta_{ac}=150$, what is the ac load output voltage.

4-What is the total output voltage of the unloaded JFET amplifier in Fig. (4). You may consider $I_{DSS}=12\text{mA}$, and $V_{GS(off)}=-3\text{V}$. If a $4.7\text{K}\Omega$ load is ac coupled to the output of the amplifier. What is the resulting peak output voltage.

5-4-For the class AB push-pull power amplifier shown in Fig. (3):

a-Determine the dc parameters $V_{B(Q1)}$, $V_{B(Q2)}$, V_E , I_{CQ1} , $V_{CE(Q1)}$, and $V_{CE(Q2)}$.

b-Assuming the peak value of the input voltage is 5V , determine the power delivered to the load resistor.

c-Draw the output waveform if: (i)capacitor C_1 opened, (ii)capacitor C_2 opened, (iii)both C_1 , and C_2 opened together.

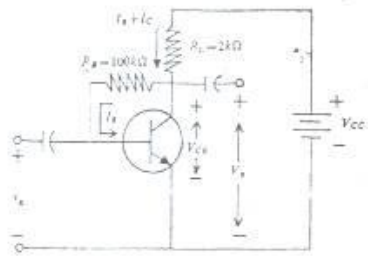


Fig.(1)

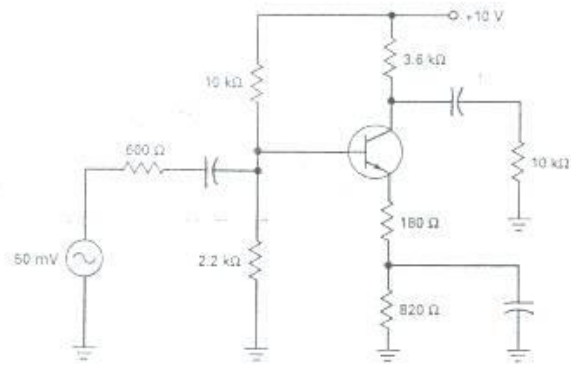


Fig.(2)

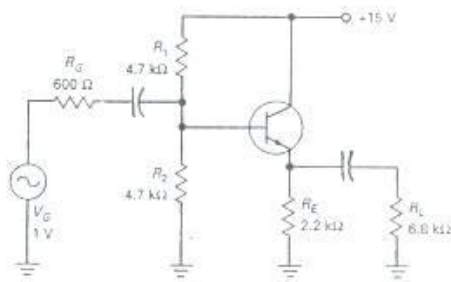


Fig.(3)

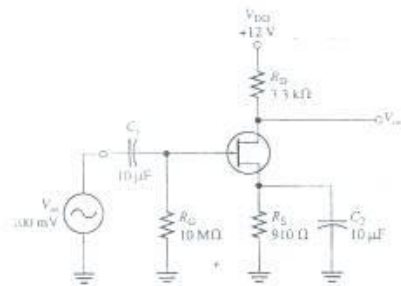


Fig.(4)

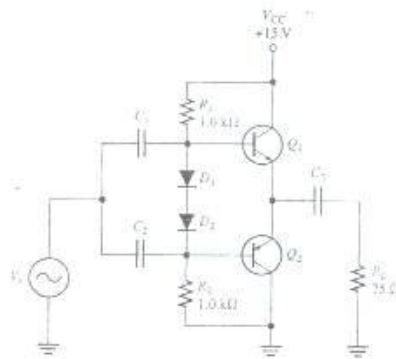


Fig.(5)

TANTA UNIVERSITY

Faculty of Engineering **Dep of Electrical Commun. Eng.**
Electronic Measurements **2nd Year- Final Term Exam.**
Date: 18/01/2007 **Time Allowed: 3 Hours**

Answer All The Following

Q1-a-A symmetrical π resistors attenuator with $R_2 = mR_1$ has a characteristic resistance R_0 and attenuation \bar{A} . Drive an expressions for the attenuator resistors.

b-A voltage divider containing two resistors R_1 , and R_2 of values $90 \text{ K}\Omega$ and $10 \text{ K}\Omega$ is used as an attenuator in an instrument. Find the voltage gain and the attenuation in decibels. If the transistor and stray capacitance C_2 across the $10 \text{ K}\Omega$ resistor is of 50 pF , find the value of C_1 across $90 \text{ K}\Omega$ resistor that compensates for C_2 .

Q2-a-Draw the circuit diagram of the bridge RC notch filter. Drive an expression for the notch frequency. Sketch the notch filter gain versus the frequency.

b-Find the pass-band gain and the cutoff frequency of a high pass RC filter with $R=100\text{K}\Omega$, $C=500\text{pF}$, $R_c=20\text{K}\Omega$, and $R_L=150 \text{ K}\Omega$.

Q3-a-Draw the block diagram of the function generator. Explain on your diagram the different output waveforms indicating the relation between their frequencies.

b-Draw the circuit diagram of the phase shift oscillator using field effect transistor and RC feedback network. Drive an expression for the oscillation frequency of the oscillator.

Q4-a-With aid of circuit diagram, explain the function of the differential amplifier. Draw it's equivalent circuit. Give an expression for the CMRR of the amplifier.

b-Construct a circuit containing a peak and a base clippers (slicer circuit) to generate a square pulses if the input to the circuit is a sinusoidal wave.

Q5-a- What are applications of an operational amplifier. With aid of circuit diagram explain how this can be used as a summer, integrator, and differentiator.

b- With aid of circuit diagram, explain the working of the wave analyzer. Drive an expressions for the deflection and maximum deflection of the dynamometer.

Technical Writing

Question 1

- 1- What are the stages of the report preparation?
- 2- What are the points required to review the rough draft of technical report
- 3- How to write references and why is required?

Question 2

- 1- What are the basic parts and subsidiary parts of a formal report?
Discuss briefly three basic parts and two subsidiary parts of them.
- 2- Write a letter to accept a job and another one to decline? it.
- 3- Write the main parts which appendix involved.

Question 3

- 1- How to write a useful abstract?
- 2- Mention the important points for a good Graphs, Drawing and?
Photographs in technical report?
- 3- How are the data presented in the results?

Question 4

- 1- What is a Spreadsheet?
- 2- What are the advantages of using a Spreadsheet?
- 3- What is the oral report?
- 4- Write the dimensions of A0, A1, A2, A3, A4, A5, A6 and applications of using it?

Attempt all questions:

- 1-a- If the base band signal $m(t) = 40 \cos(2\pi \cdot 10^4 t)$ is used to modulate the carrier $100 \cos(2\pi \cdot 10^6 t)$ via **DSB-TC system**
- (1) Write down an expression for and sketch the time domain of the modulated signal.
 - (2) Sketch the spectrum of the modulated signal as well as its power spectral density
 - (3) Evaluate the total transmitted power and deduce the transmission B.W, and evaluate the modulation efficiency
 - (4) Draw and explain briefly the operation of the **modulator and demodulator**
- b- Repeat the above required in (a) for the **SSB-SC** case
- c- Aided with the circuit diagram, explain the operation of both the **ring modulator and the envelope detector**.
- d- Make a comparison between the different AM techniques:
- e- If the signal $m(t)$ is used to modulate the carrier $200 \cos(2\pi \cdot 10^6 t)$ via **SSB-TC** technique and the transmitted power is 20.8 kw. Evaluate the transmitted power if the same signal is used to modulate the carrier $80 \cos(2\pi \cdot 10^7 t)$ via **DSB-TC**
-
- 2- a- Draw the block diagram of the **F.D.M system** for the transmission and reception of the following signals and estimate the required B.W:
- i- $m_1(t) = 8 \cos(2\pi \cdot 10^4 t)$ with a carrier $80 \cos(2\pi \cdot 10^6 t)$ (standard AM)
 - ii- $m_2(t) = 6 \cos(2\pi \cdot 5 \cdot 10^4 t)$ with a carrier $60 \cos(2\pi \cdot 2 \cdot 10^6 t)$ (DSB-SC)
 - iii- $m_3(t) = 4 \cos(2\pi \cdot 8 \cdot 10^4 t)$ with a carrier $40 \cos(2\pi \cdot 4 \cdot 10^6 t)$ (SSB-SC)
- b- Draw the block diagram of the super – heterodyne receiver indicating the signal spectrum at the output of each block when receiving an AM broadcasting signal modulating the carrier $A_c \cos(1.8\pi \cdot 10^6 t)$.
-
- 3-a- An angle modulated signal is given by:
- $$V(t) = 10 \cos(2\pi \cdot 10^3 t + 4 \sin(2\pi \cdot 10^4 t))$$
- (1) If the signal is an **FM signal** with $k_{FM} = 2\pi \cdot 10^3$ rad /sec/volt, deduce the modulating signal $g(t)$ and calculate the maximum frequency and phase deviations, $((\Delta\omega)_{\max})$ and $((\Delta\phi)_{\max})$, and deduce the required BW.
 - (2) Repeat the above required in (1) if the signal is an **PM signal** with $k_{PM} = 2$ rad /volt
- b- For the **NBFM system**: Write down an expression for the time domain of the modulated signal indicating the condition required to ensure the NBFM case and the required BW and draw the block diagram of both the modulator and demodulator of the system.
-
- 4- a- Draw the block diagram concerning the indirect method for FM generation (**Armstrong method**)
- b- If the above modulator is used to transmit a single tone signal with $f_m = 20$ KHz and the modulation index of the NBFM modulator is 0.2 while its crystal controlled oscillator frequency is 400 KHz. The used mixer is supplied with a crystal oscillator whose frequency is $f_c = 5$ MHz. What are the values of the frequency multipliers **N1 and N2** that result in an output WBFM signal with carrier frequency $f_{co} = 40$ MHz. and a maximum frequency deviation of 200 KHz
- c- Explain briefly how to generate the FM signal using the variable capacitor method.
- d- Aided with the block diagram, explain how to demodulate the FM signal using the **feed back method indicating the function of frequency discriminator** aided with its circuit diagram. What are the main advantages of this method.

أسامة أحمد إبراهيم
دوائر الترددية (1)

Tanta University
Faculty of Engineering
Electronics & Comm. Dept.
Second Year

Final Term Examination
Course : Electronic Circuits (2)
Time : 3 Hours
Date : -1-2006

هندسة طباطبانات

Answer All Questions

1-a) Given the information provided in Figure 1a, determine R_C , R_E , R_B , V_{CE} , and V_B [$\beta=100$].

b) Given the information provided in Figure 1b, determine I_C , I_E , V_{CE} , V_{CB} , V_{BE} , and R_i [$\beta=100$].

2-a) What is the significant difference between the construction of an enhancement MOSFET and a depletion type MOSFET.

b) Determine V_{GSQ} , I_{DQ} , V_{DS} , V_S , V_G , V_D for the circuit shown in Figure 2b. The data sheet gives $I_{DSS} = 8\text{mA}$, $V_P = 6\text{V}$.

3-a) Determine V_{GSQ} , I_{DQ} , V_{DS} , V_S , V_G , V_D for the circuit shown in Figure 3a. The data sheet gives $I_{DSS} = 12\text{mA}$, $V_P = 6\text{V}$.

b) Determine V_{GSQ} , I_{DQ} , V_D for the circuit shown in Figure 3b. The data sheet gives $I_{DSS} = 8\text{mA}$, $V_P = 8\text{V}$.

4-a) Redraw the network of Figure 4a for the ac response with r_e model and hybrid model

b) For the circuit shown in Figure 4b, determine r_e , Z_i , Z_o , and A_v .

5) For the circuit shown in Figure 5, determine r_e , Z_i , Z_o , A_i , and A_v .

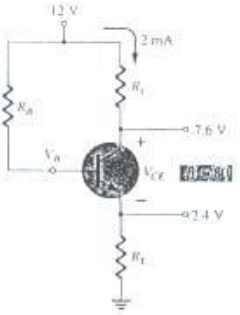


Fig. 1a

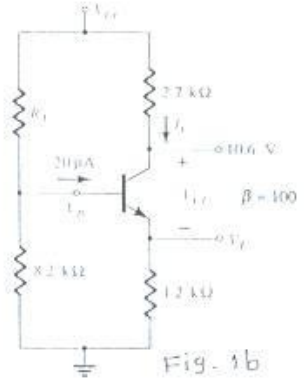


Fig. 1b

